#### Dana tabela przejść automatu

$S \setminus X_1 X_0$	00	01	11	10
S <sub>1</sub>	$S_2$	$S_3$	S <sub>1</sub>	$S_2$
$S_2$	$S_3$	S <sub>1</sub>	$S_4$	$S_4$
$S_3$	$S_2$	$S_4$	S <sub>1</sub>	S <sub>3</sub>
$S_4$	S <sub>1</sub>	$S_4$	$S_2$	S <sub>4</sub>

 $S_1 = 01$ 

$S \setminus X_1 X_0$	00	01	11	10
01	$S_2$	S <sub>3</sub>	01	$S_2$
$S_2$	$S_3$	01	$S_4$	S <sub>4</sub>
$S_3$	$S_2$	$S_4$	01	$S_3$
S <sub>4</sub>	01	$S_4$	$S_2$	S <sub>4</sub>

 $S_2 = 11$ 

$S \setminus X_1 X_0$	00	01	11	10
01	11	S <sub>3</sub>	01	11
11	$S_3$	01	$S_4$	$S_4$
$S_3$	11	$S_4$	01	S <sub>3</sub>
S <sub>4</sub>	01	$S_{\scriptscriptstyle{4}}$	11	$S_4$

$$S_3 = 00$$

$S \setminus X_1 X_0$	00	01	11	10
01	11	00	01	11
11	00	01	$S_4$	$S_4$
00	11	$S_4$	01	00
S <sub>4</sub>	01	$S_4$	11	$S_4$

 $S_4 = 10$ 

$S \setminus X_1 X_0$	00	01	11	10
01	11	00	01	11
11	00	01	10	10
00	11	10	01	00
10	01	10	11	10

### Uporządkowana tabela przejść

$S \setminus X_1 X_0$	00	01	11	10
00	11	10	01	00
01	11	00	01	11
11	00	01	10	10
10	01	10	11	10

#### Mapy Karnaugh'a funkcji wzbudzeń przerzutników typu D

				(	$Q_1Q_0 \setminus X_1X_0$	00	01	11	10	
					00	1	0	1	0	
					01	1	0	1	1	
$Q_1Q_0 \setminus X_1X_0$	00	01	11	10	11	0	1	0	0	
00	11	10	01	00	10	1	0	1	0	
01	11	00	01	11	$Q_1Q_0 \setminus X_1X_0$	00	01	11	10	$D_0$
11	00	01	10	10						
10	01	10	11	10	00	1	1	0	0	
					01	1	0	0	]	
					11 10	0	0 1	1	1	
										$D_1$

#### Mapy Karnaugh'a funkcji wzbudzeń przerzutników typu T

 $Q_1 Q_0 \setminus X_1 X_0 = 00$ 

10

					00	1	0	]
					01	0	1	0
$Q_1Q_0 \setminus X_1X_0$	00	01	11	10	11	1	0	1
					10	1	0	1
00	11	10	01	00				
01	11	00	01	11	$Q_1Q_0 \setminus X_1X_0$	00	01	11
11	00	01	10	10	00	1	1	0
10	01	10	11	10		'	•	J
					01	1	0	0
					11	1	1	0

 $T_0$ 

10

10

 $T_1$ 

# Wzbudzenia przerzutnika Q<sub>0</sub>

$Q_{1}Q_{0} \setminus X_{1}X_{0}$	00	01	11	10
00	11	10	01	00
01	11	00	01	11
11	00	01	10	10
10	01	10	11	10

6	$Q_1 Q_0 \setminus X_1 X_0$	00	01	11	10	$J_{0}$
	00	1	0	1	0	
	01	-	-	-	-	
	11	-	-	-	-	
Ì	10	1	0	1	0	
		1				ı

$Q_1Q_0 \setminus X_1X_0$	00	01	11	10
00	-	-	-	-
01	0	1	0	0
11	1	0	1	1
10	-	-	-	-

## Wzbudzenia przerzutnika Q<sub>1</sub>

Q	$Q_0 \setminus X_1 X_0$	00	01	11	10	
	00	11	10	01	00	
	01	11	00	01	11	(
	11	00	01	10	10	
	10	01	10	11	10	

(	$Q_1Q_0 \setminus X_1X_0$	00	01	11	10	$\mathbf{J}_{_{1}}$
	00	1	1	0	0	
	01	1	0	0	1	
	11	-	-	-	-	
	10	-	-	-	-	
)		1				
	$Q_1Q_0 \setminus X_1X_0$	00	01	11	10	

$Q_1Q_0 \setminus X_1X_0$	00	01	11	10	$\nu$
00	-	-	-	-	K <sub>1</sub>
01	-	-	-	-	
11	1	1	0	0	
10	1	0	0	0	

# Wzbudzenia przerzutnika Q<sub>0</sub>

$Q_1Q_0 \setminus X_1X_0$	00	01	11	10
$\alpha^{1}\alpha^{0} / \gamma^{1}\gamma^{0}$	00	01	1 1	10
00	11	10	01	00
01	11	00	01	11
11	00	01	10	10
10	01	10	11	10

$Q_1 Q_0 \setminus X_1 X_0$	00	01	11	10	$R_{\scriptscriptstyle 0}$
00	0	-	0	-	
01	0	1	0	0	
11	1	0	1	1	
10	0	-	0	-	
	1				ı

$Q_1Q_0 \setminus X_1X_0$	00	01	11	10	
00	1	0	1	0	;
01	-	0	-	-	
11	0	-	0	0	
10	1	0	1	0	

### Wzbudzenia przerzutnika Q<sub>1</sub>

$Q_1 Q_0 \setminus X_1 X_0$	00	01	11	10
00	11	10	01	00
01	11	00	01	11
11	00	01	10	10
10	01	10	11	10

(	$Q_1 Q_0 \setminus X_1 X_0$	00	01	11	10	$R_{_{1}}$
	00	0	0	-	-	
	01	0	-	-	0	
	11	1	1	0	0	
	10	1	0	0	0	
	$Q_1Q_0 \setminus X_1X_0$	00	01	11	10	$\mathbf{S}_{1}$
	00	1	1	0	0	
١						1

#### Ogólna struktura automatów synchronicznych



